


A futuristic robot arm, white and black, reaches out from the left side of the frame. The background is a composite image featuring a row of server racks on the right, a series of DNA double helices on the left, and a purple band across the center. The text 'ELEC1100: Introduction to Electro-Robot Design' is overlaid on the purple band.

ELEC1100: Introduction to Electro-Robot Design

Lecture 11: Logics



ELEC1100 ROADMAP

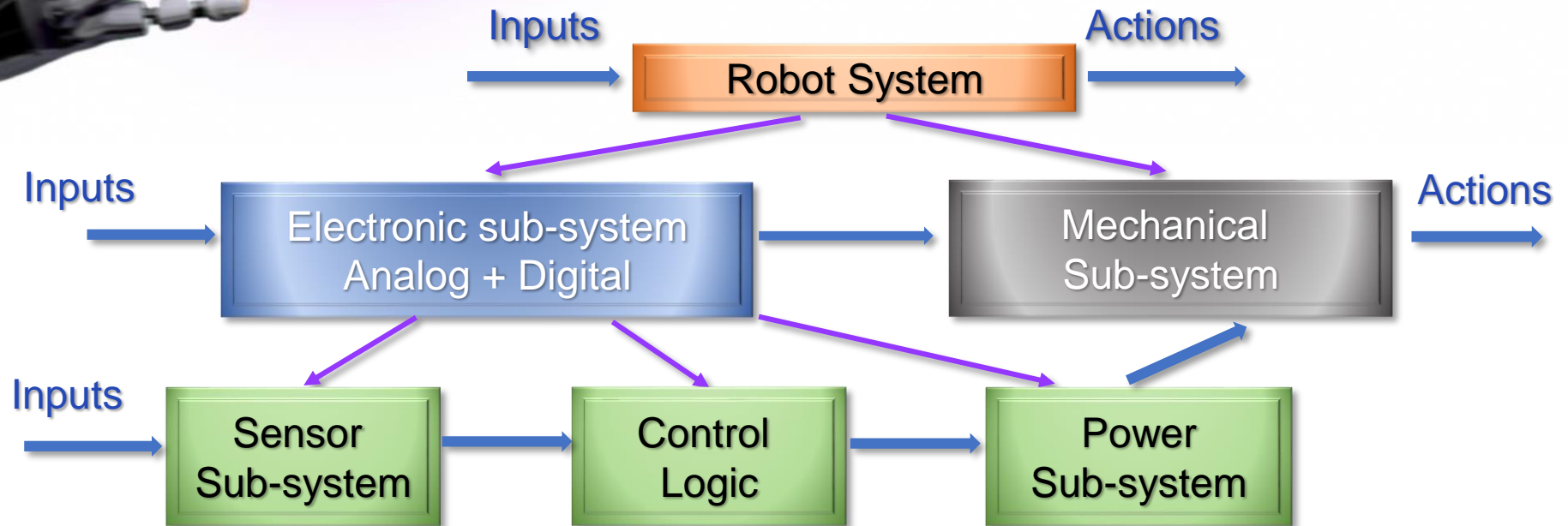

Sensor Basics:

Wk5: Sensor Basic –
Sensor/Line/ADC

Combinational/Sequential Logic:

Wk6: Robot Brain: Logic Gate and
Logic Operation

Basic electronics:

Wk1: Basic Electronics -
Charge/Current/Voltage/Resistor
Wk2: Energy/Power and DC Sources

Motor Power Supply:

Wk3: Pulse Signal and PWM Control
Wk4: Transistor and H-Bridge





BINARY NUMBER

- ❖ Decimal number system – base 10, each digital is selected from the set $\{0,1,2,3,4,5,6,7,8,9\}$
- ❖ Binary number system – base 2, each digital is selected from the set $\{0,1\}$

Multiplication and addition of binary number						
+	0	1		*	0	1
0	0	1		0	0	0
1	1	0		1	0	1

Base 10	Base 2
0	0000
1	0001
2	0010
3	0011
4	0100
5	0101
6	0110
7	0111
8	1000
9	1001
10	1010





BINARY NUMBER OPERATION

❖ Addition

Decimal	Binary
7	0111
+ 5	+ 0101
<hr/>	
12	1100

❖ Multiplication

Decimal	Binary	
7	0111	
× 5	× 0101	
<hr/>		
35	0111	
	0111	
	<hr/>	
	100011	

- ❖ Binary digit: 0 and 1 can be represented by logic (True or False)
 - 0 is equivalent to False
 - 1 is equivalent to True
- ❖ Use Boolean Algebra (which operates on {T,F}) to manipulate the binary digit operation





LOGIC GATES


- ❖ Two values for logic: True (“T”) and False (“F”)
- ❖ A logic input can be combined with another logic input in different ways to form a new logic output. We call this combination of the inputs as logic gates.
- ❖ There are seven fundamental logic gates:
 - Inverter (Not) – 1 input, 1 output
 - AND – 2 or more inputs, 1 output
 - NAND – 2 or more inputs, 1 output
 - OR – 2 or more inputs, 1 output
 - NOR – 2 or more inputs, 1 output
 - XOR – 2 or more inputs, 1 output
 - XNOR – 2 or more inputs, 1 output





TRUTH TABLE

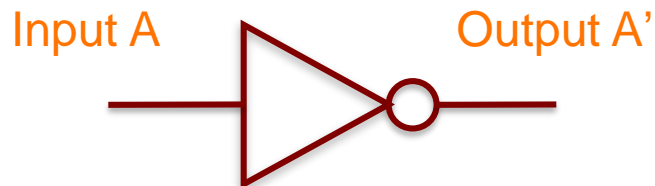- ❖ A tabular summary for all the possible outputs of a logic gate, given all the possible input values
- ❖ For a logic gate that has n inputs, how many possible input combinations do we have?
- ❖ Sometimes we use 0 to represent F and 1 to represent T
- ❖ Truth table of an inverter



Input A	Output A'
0	1
1	0



AND/OR GATES


❖ AND gate: $\text{Output} = A \cdot B$



A	B	Output
0	0	0
0	1	0
1	0	0
1	1	1

e.g. if tmr is sunny and I finish ELEC 1100 hw, I'll go hiking.


❖ OR gate: $\text{Output} = A + B$

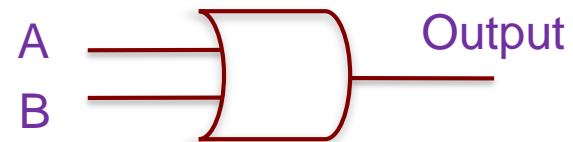

A	B	Output
0	0	0
0	1	1
1	0	1
1	1	1

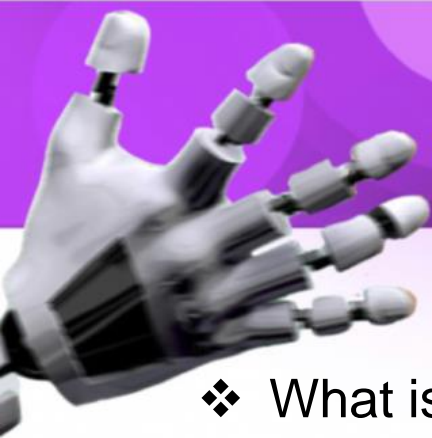
e.g. if it rains tmr or I cannot finish ELEC 1100 hw, I'll stay home.





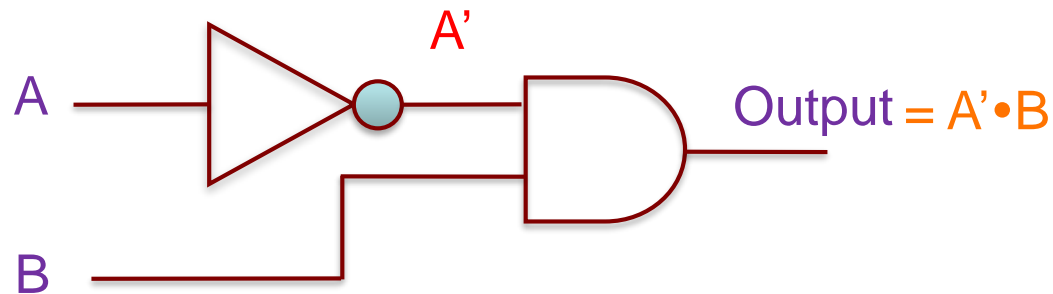EXAMPLE OF CIRCUIT WITH AND GATE

- ❖ What is the output logic expression for the circuit below?





- ❖ Complete the truth table

A	B	A'	Output
0	0	1	0
0	1	1	1
1	0	0	0
1	1	0	0





MORE EXAMPLE (AND GATE)

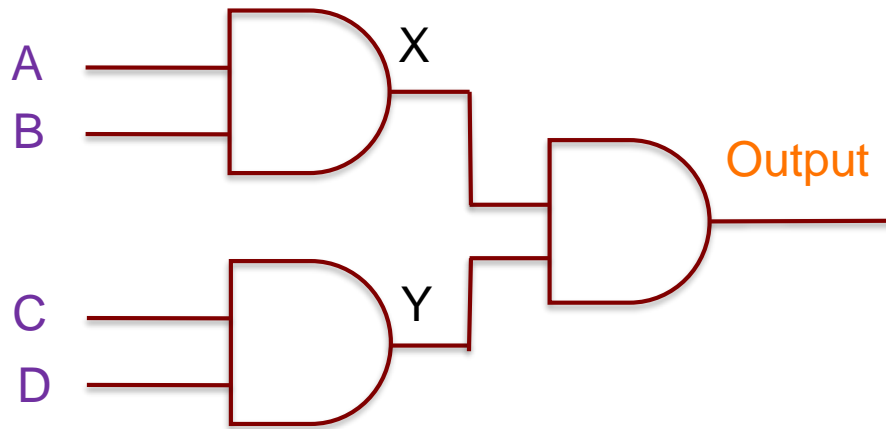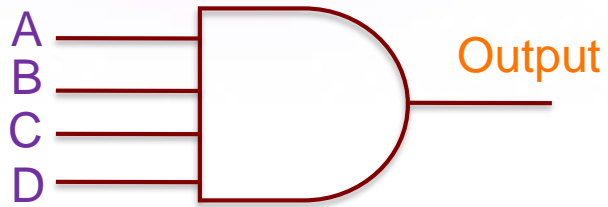



4-input AND gate

A	B	C	D	Output
0	0	0	0	0
0	0	0	1	0
0	0	1	0	0
0	0	1	1	0
0	1	0	0	0
0	1	0	1	0
0	1	1	0	0
0	1	1	1	0
1	0	0	0	0
1	0	0	1	0
1	0	1	0	0
1	0	1	1	0
1	1	0	0	0
1	1	0	1	0
1	1	1	0	0
1	1	1	1	1





MORE EXAMPLE (OR GATE)

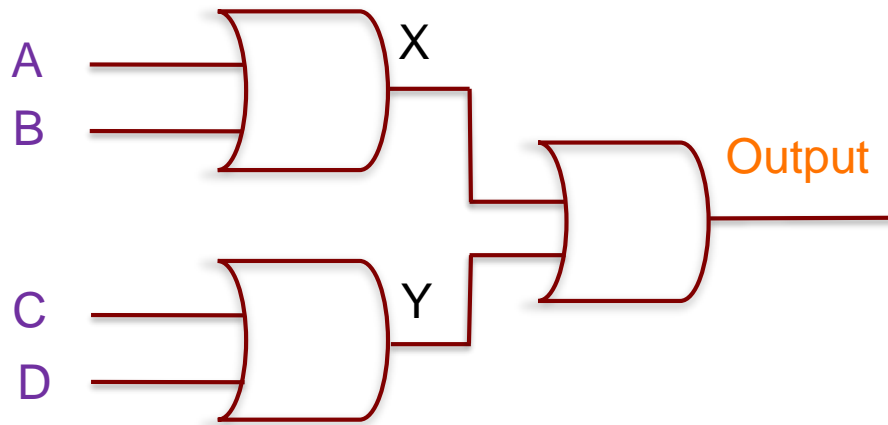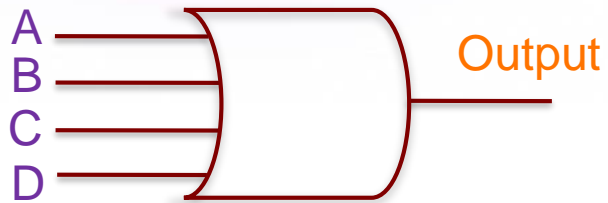

4-input OR gate

A	B	C	D	Output
0	0	0	0	0
0	0	0	1	1
0	0	1	0	1
0	0	1	1	1
0	1	0	0	1
0	1	0	1	1
0	1	1	0	1
0	1	1	1	1
1	0	0	0	1
1	0	0	1	1
1	0	1	0	1
1	0	1	1	1
1	1	0	0	1
1	1	0	1	1
1	1	1	0	1
1	1	1	1	1






NAND/NOR GATES

❖ NAND gate: **Output = $\overline{A \cdot B}$**



A	B	Output
0	0	1
0	1	1
1	0	1
1	1	0








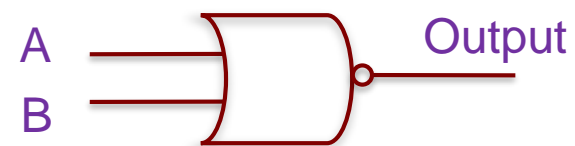
❖ NOR gate: **Output = $\overline{A + B}$**



A	B	Output
0	0	1
0	1	0
1	0	0
1	1	0



SOME EQUIVALENT GATES

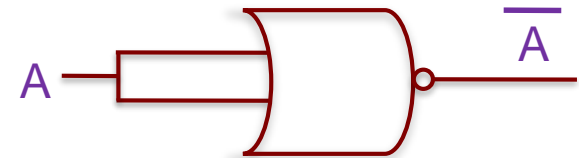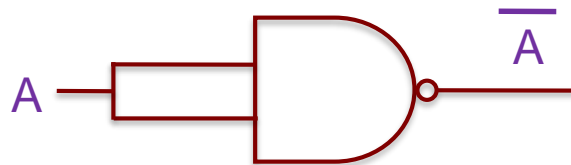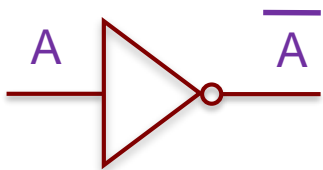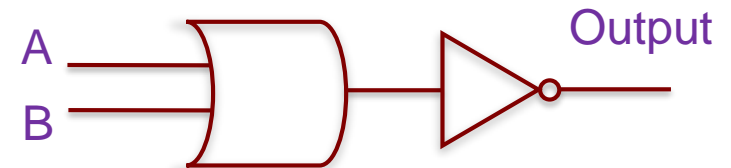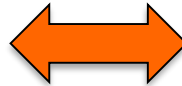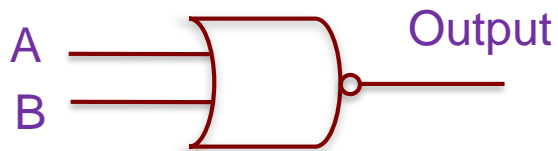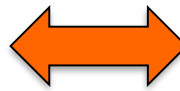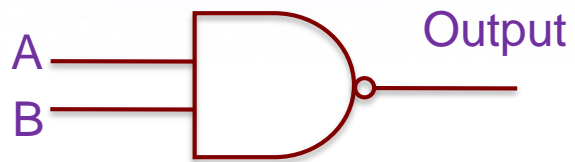



XOR/XNOR GATES

❖ XOR gate: $\text{Output} = A \oplus B$



A	B	Output
0	0	0
0	1	1
1	0	1
1	1	0

❖ XNOR gate: $\text{Output} = \overline{A \oplus B}$



A	B	Output
0	0	1
0	1	0
1	0	0
1	1	1



LAW OF BOOLEAN ALGEBRA

- $0 + X = X$
- $1 + X = 1$
- $X' + X = 1$
- $0 \cdot X = 0$
- $1 \cdot X = X$
- $X \cdot X = X$
- $X \cdot X' = 0$
- $(X')' = X$

❖ Exchange:

- $X + Y = Y + X$
- $X \cdot Y = Y \cdot X$

❖ Associativity:

- $X + (Y + Z) = (X + Y) + Z$
- $X \cdot (Y \cdot Z) = (X \cdot Y) \cdot Z$

❖ Distributivity

- $X \cdot (Y + Z) = X \cdot Y + X \cdot Z$

❖ DeMorgan's Law

- $(X + Y)' = X' \cdot Y'$
- $(XY)' = X' + Y'$





LOGIC SIMPLIFICATION

➤ $X + X \cdot Z = X$

$$X + X \cdot Z = X \cdot (1 + Z) = X$$

➤ $X \cdot (X + Y) = X$

$$X \cdot (X + Y) = X \cdot X + X \cdot Y = X \cdot (1 + Y) = X$$

➤ $(X + Y) \cdot (X + Z) = X + Y \cdot Z$

$$(X + Y) \cdot (X + Z) = X \cdot X + X \cdot Z + Y \cdot X + Y \cdot Z = X \cdot (1 + Z + Y) + Y \cdot Z = X + Y \cdot Z$$

➤ $X' + XY = X' + Y$

$$X' + XY = (X \cdot (XY)')' = (X \cdot (X' + Y'))' = (X \cdot Y')' = X' + Y$$

➤ $(XY)' + (YZ)' + (XZ)' = (XY)' + (XZ)'$


$$(XY)' + (YZ)' + (XZ)' = (X' + Y') + (Y' + Z') + (X' + Z') = (XY)' + (XZ)'$$





VOLTAGE AND LOGIC VALUE

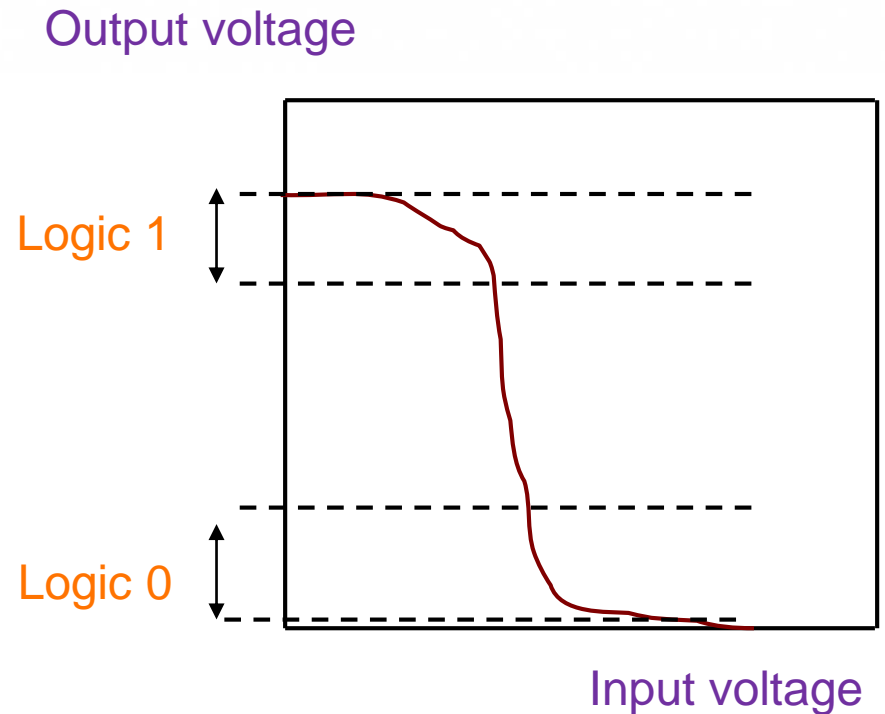
- ❖ How do we represent binary digital signals?
- ❖ We can use a range of voltage values to represent logic 0 or 1
- ❖ Sometimes we just use high voltage to represent 1 and low voltage to represent 0





LOGIC GATE CONSTRUCTION WITH DIODES [1]

❖ AND gate

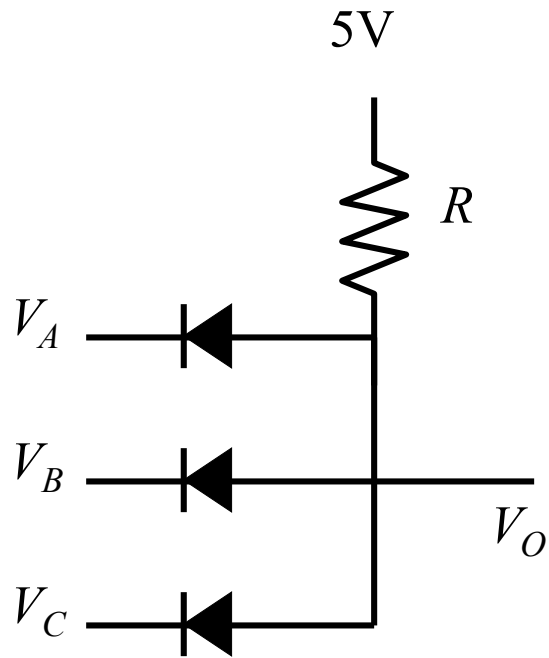

Input/Output Table

V_A	V_B	V_C	V_O
0	0	0	0
0	0	1	0
0	1	0	0
0	1	1	0
1	0	0	0
1	0	1	0
1	1	0	0
1	1	1	1

1 = 5V


0 = 0V



LOGIC GATE CONSTRUCTION WITH DIODES

[2]

❖ OR gate

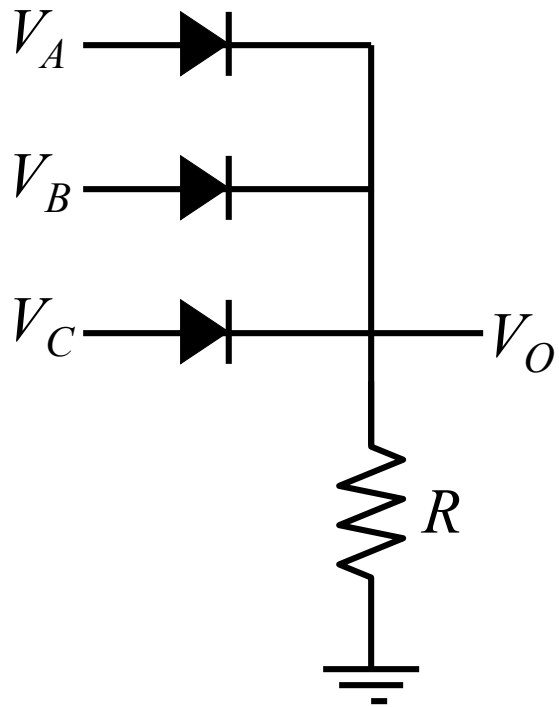

Input/Output Table

V_A	V_B	V_C	V_O
0	0	0	0
0	0	1	1
0	1	0	1
0	1	1	1
1	0	0	1
1	0	1	1
1	1	0	1
1	1	1	1

1 = 5V

0 = 0V












LECTURE SUMMARY

❖ Binary digit: 0 and 1 can be represented by logic (True or False)

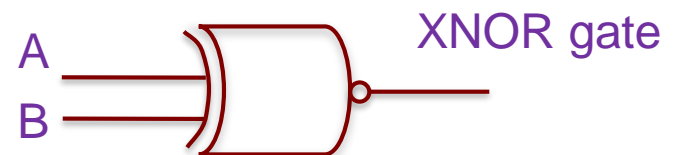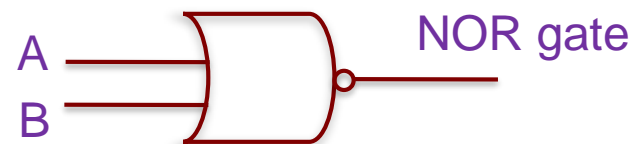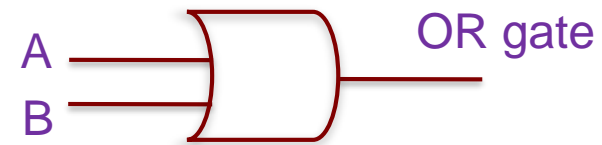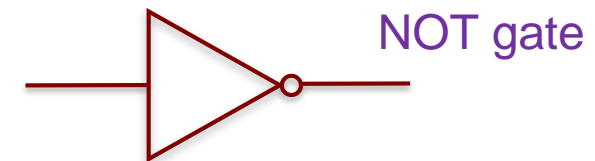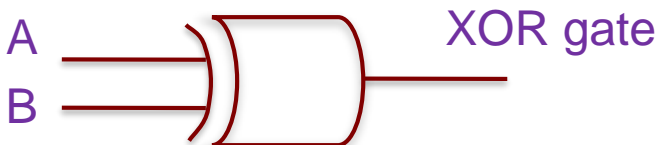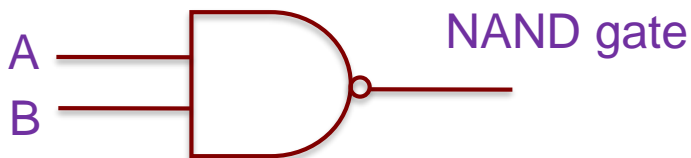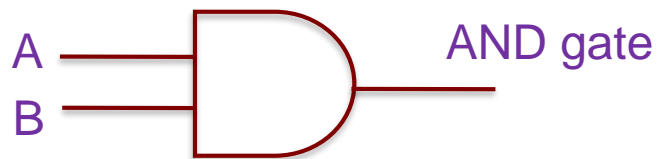- 0 is equivalent to False
- 1 is equivalent to True





NEXT LECTURE

- ❖ K-map
- ❖ K-map simplification



QUESTIONS?

